

# 11.3 Capacitance


## Question Paper

Course	DPIB Physics
Section	11. Electromagnetic Induction (HL only)
Topic	11.3 Capacitance
Difficulty	Hard

**Time allowed:** 60  
**Score:** /46  
**Percentage:** /100

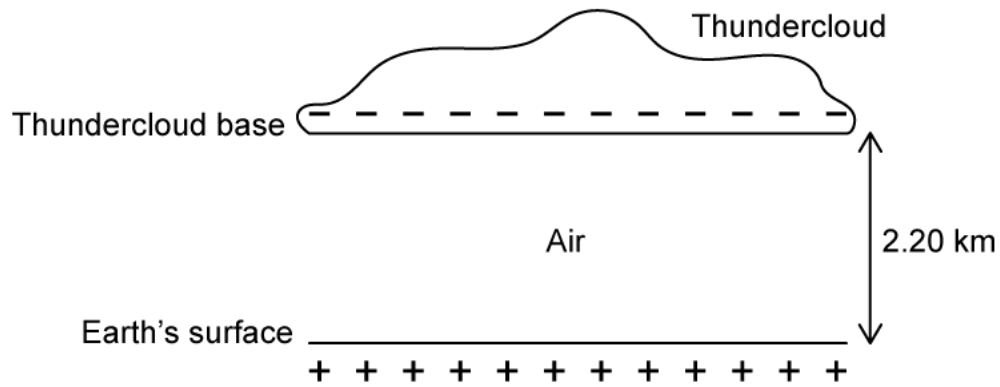**Question 1a**

A thundercloud is 2.20 km above the surface of Earth. The charge on the base of the cloud is  $-30.0\text{ C}$ . The air between the cloud and the Earth is humid and rainy, making it 4.35 % water by mass.



The relative permittivity for a homogenous mixed medium,  $\epsilon_{r(m)}$ , is given by:

$$\epsilon_{r(m)} = \phi_1 \epsilon_{r(1)} + \phi_2 \epsilon_{r(2)}$$

Where  $\epsilon_{r(1)}$  &  $\epsilon_{r(2)}$  represent the relative permittivities of each material in the mixture and  $\phi_1$  &  $\phi_2$  represent the fraction by mass of each material.

The permittivity of water is  $7.08 \times 10^{-10}\text{ F m}^{-1}$  and the permittivity of air is  $8.85 \times 10^{-12}\text{ F m}^{-1}$ .

(a)

Show that the dielectric constant of the rainy air is about 4.

[4]

[4 marks]

**Question 1b**

The cloud has a roughly rectangular base of length 5.00 km and the potential difference from the base of the cloud to Earth is  $-8.00 \times 10^8$  V.

(b)

Calculate the width of the cloud.

[3]

[3 marks]

**Question 1c**

Lightning strikes a tree after strong winds increase the potential difference of the system to  $-9.0 \times 10^9$  V. Air conducts electricity once there is a potential difference of  $3.00 \times 10^6$  V per metre.

(c)

Given that, in a storm, the rainy air has a resistance of  $136 \Omega \text{ m}^{-1}$ , determine the time period of the lightning strike.

Assume the cloud's area and distance from the ground are unchanged by the wind.

[4]


[4 marks]

### Question 2a

A tattoo removal company uses a pulsed Nd:YAG laser used a capacitor to store energy and produce a short laser pulse. When pulses in the nanosecond range are discharged, tattoo pigments are removed without damaging skin cells.

The research and design team of a company that produces these lasers are experimenting with different dielectrics in the capacitor. One suggestion is to use a cubic dielectric material that is half glass, with permittivity  $\epsilon_G$ , and half silicon, with permittivity  $\epsilon_{Si}$ , split down the middle.

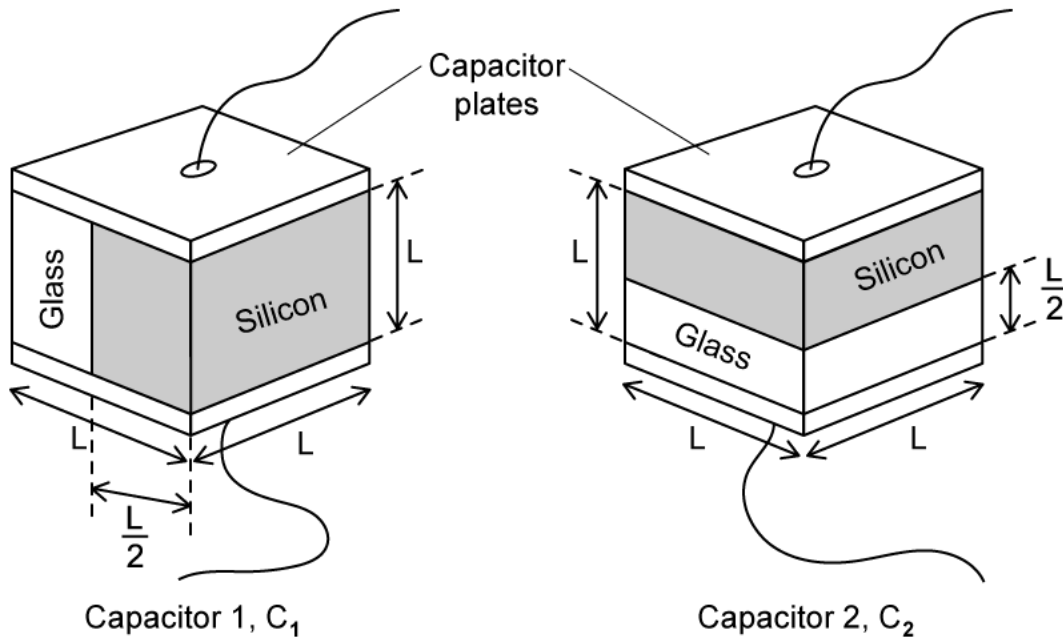This mixed medium is used in two orientations during tests.



The capacitor with the dielectric split vertically has a capacitance of  $C_1$  and the capacitor with the dielectric split down the middle has a capacitance of  $C_2$ .

(a)

Write an expression for capacitance,  $C_1$ , in terms of  $L$ ,  $\epsilon_G$  and  $\epsilon_{Si}$ .

[3]

[3 marks]

### Question 2b

(b)

Write an expression for capacitance,  $C_2$ , in terms of  $L$ ,  $\epsilon_G$  and  $\epsilon_{Si}$ .

[4]

[4 marks]

### Question 2c

Capacitor 1 and capacitor two are connected in two different circuits. The charge on capacitor 1 is twice that of capacitor 2.

The dielectric constant of the silicon is 4.3 and the relative permittivity of the glass is 6.5

(c)

Show that the energy stored in capacitor 2 is 26 % of the energy stored in capacitor 1.

(i)

Show that  $\frac{E_2}{E_1} = \frac{(\epsilon_{Si} + \epsilon_G)^2}{16\epsilon_G\epsilon_{Si}}$ , where  $E_n$  is the energy stored in capacitor  $n$  and  $\epsilon_z$  is the permittivity of material  $z$ .

[3]

(ii)

Calculate  $E_2$  as a percentage of  $E_1$ .

[2]

[6 marks]

### Question 3a


A capacitor with capacitance  $220 \mu\text{F}$  is attached to an ac voltage source which provides a voltage which varies according to the following equation:

$$V = V_0 \sin(\omega t)$$

The rate of change of the voltage is given by:

$$\frac{\Delta V}{\Delta t} = \omega V_0 \cos(\omega t)$$

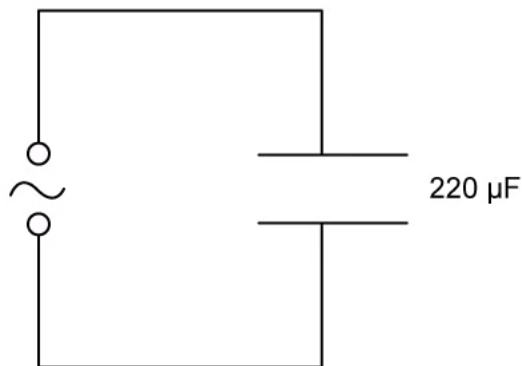This circuit is called 'purely capacitive', meaning that resistance can be assumed to be zero.



The power supply is adjusted such that the initial voltage is  $6.0 \text{ V}$  and the alternating voltage frequency is  $4000 \text{ rad s}^{-1}$ .

(a)


Calculate the magnitude of the current flowing in the circuit at time  $t = 3.14 \text{ s}$ .

[4]

[4 marks]
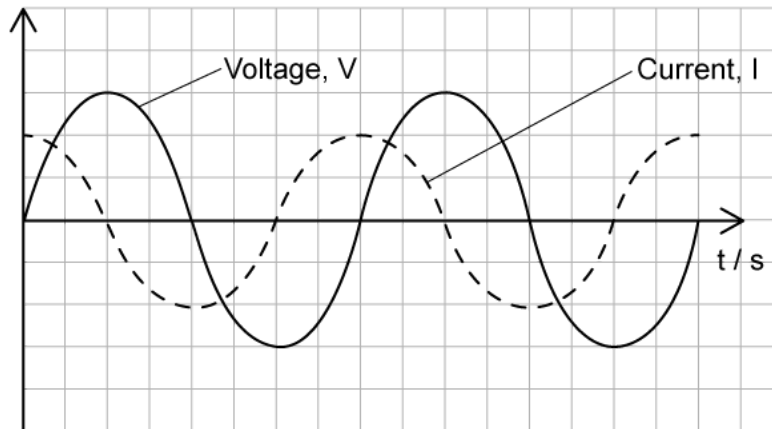
### Question 3b

The variation of voltage  $V$  and current  $I$  in the circuit is shown.



(b)

Discuss the phase difference between the variation of  $V$  and  $I$  in the circuit.

[3]

[3 marks]

**Question 3c**

'Capacitive reactance'  $X$  is the opposition to current flow in a purely capacitive circuit as described in part (a). Capacitive reactance is comparative to resistance, in that it is measured by the same units  $\Omega$ .

(c)

By considering the ratio of the maximum voltage and current in the circuit, show that the capacitive reactance  $X$  is given by

$$X = \frac{1}{\omega C}$$

and verify that  $X$  has the same units as resistance.


[4]

[4 marks]




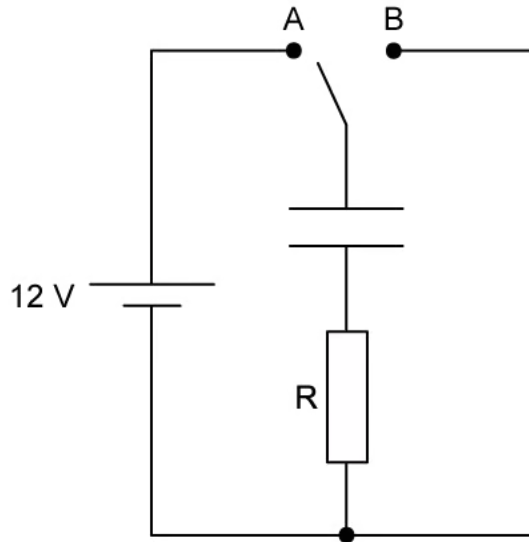**Question 4a**

A vacuum capacitor is connected, along with a resistor, to a cell with an emf of 12 V in the configuration below. In a vacuum, the capacitor has a capacitance of  $4.5 \mu\text{F}$ .



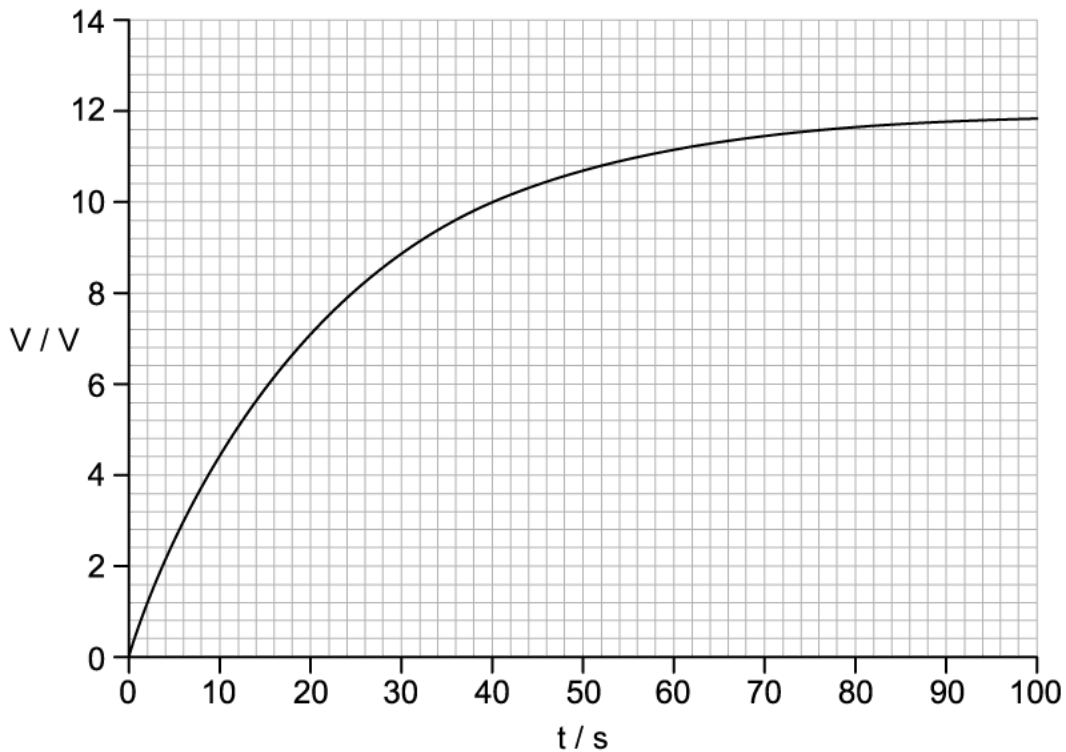Initially, the vacuum capacitor is uncharged. At a time of  $t = 0$  s, the switch is placed at position A. The voltage across the capacitor is recorded over time and plotted in the graph below.



(a)

Sketch a second line on the axes, showing the variation in the voltage across the resistor over time.

[2]

[2 marks]

### Question 4b

(b)

Using the graph, calculate the resistance,  $R$ , of the resistor.

[3]

[3 marks]

### Question 4c

The vacuum chamber is now filled with acetone, which has a dielectric constant of 19.5.

(c)

Calculate the new charge stored in the capacitor when the voltage across the capacitor is half its maximum value.

[3]

[3 marks]

### Question 4d

(d)

Once the capacitor is fully charged, the switch in the diagram in part (a) changes to position B.

(i)

Describe the energy changes in the capacitor.

[1]

(ii)

Explain why these energy changes occur.

[2]

**[3 marks]**